

Topic 5
Node Voltage Method

Node Voltage Method or point analysis

The node voltage method of analysis solves for unknown voltages at circuit nodes in terms of a system of KCL equations.

Let's use this circuit (Fig. 3) to illustrate the method:

There must be -----

- 1. Node**
- 2. Connection between nodes through branch**

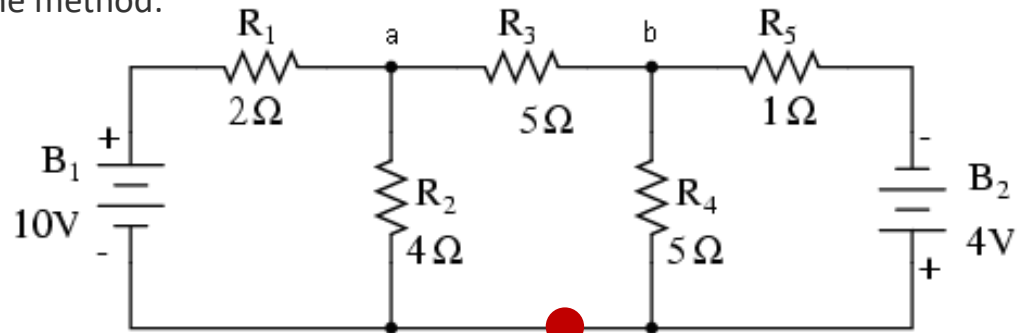


Figure 3 Reference node

Apply KCL to

Node a:

$$V_a \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

Directly connected resistors to the node
i.e. R_1, R_2, R_3

Fixed -ve

$$- \frac{V_b}{R_3}$$

Relation with other nodes
i.e. node b

**Entering I to node -ve
Leaving I from node +ve**

$$- \frac{10}{R_1} = 0$$

Enter/leave current to/from the node
i.e. current due to B_1 and R_1

Applying KCL at node 'a'

$$V_a \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{V_b}{R_3} - \frac{10}{R_1} = 0$$

$$V_a \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{5} \right) - \frac{V_b}{5} - \frac{10}{2} = 0$$

$$19V_a - 4V_b = 100 \text{ ----- Equ}^n (1)$$

Applying KCL at node 'b'


$$V_b \left(\frac{1}{R_5} + \frac{1}{R_4} + \frac{1}{R_3} \right) - \frac{V_a}{R_3} + \frac{4}{R_5} = 0$$

$$V_b \left(\frac{1}{1} + \frac{1}{5} + \frac{1}{5} \right) - \frac{V_a}{5} + \frac{4}{1} = 0$$

$$V_a - 7V_b = 20 \text{ ----- Equ}^n (2)$$

Matrix format
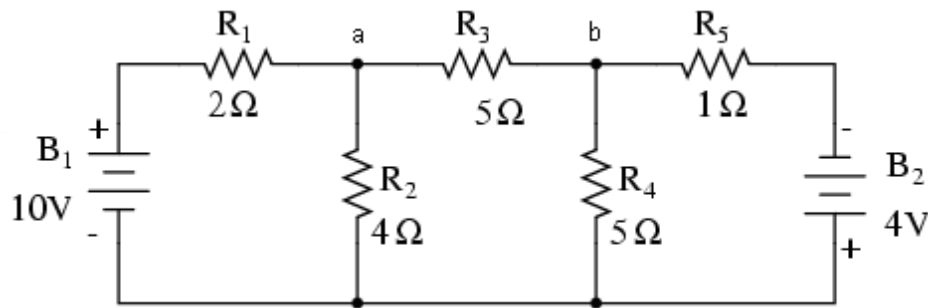
$$\begin{vmatrix} 19 & -4 \\ 1 & -7 \end{vmatrix} = \begin{vmatrix} 100 \\ 20 \end{vmatrix}$$



Substituting equⁿ (1) & (2) we have,

$$D = \begin{vmatrix} 19 & -4 \\ 1 & -7 \end{vmatrix} = -133 + 4 = -129$$

$$V_a = \frac{\begin{vmatrix} 100 & -4 \\ 20 & -7 \end{vmatrix}}{-129} = \frac{-700 + 80}{-129} = 4.81V$$

$$V_b = \frac{\begin{vmatrix} 19 & 100 \\ 1 & 20 \end{vmatrix}}{-129} = \frac{380 - 100}{-129} = 2.17V$$

$$I_1 = \frac{V_a - B_1}{R_1}; \quad I_2 = \frac{V_a}{R_2}; \quad I_3 = \frac{V_a - V_b}{R_3};$$

$$I_4 = \frac{V_b}{R_4}; \quad I_5 = \frac{V_b - B_2}{R_5}$$

Problem-1: Determine the currents through and voltages across each branch of the network using node voltage method

